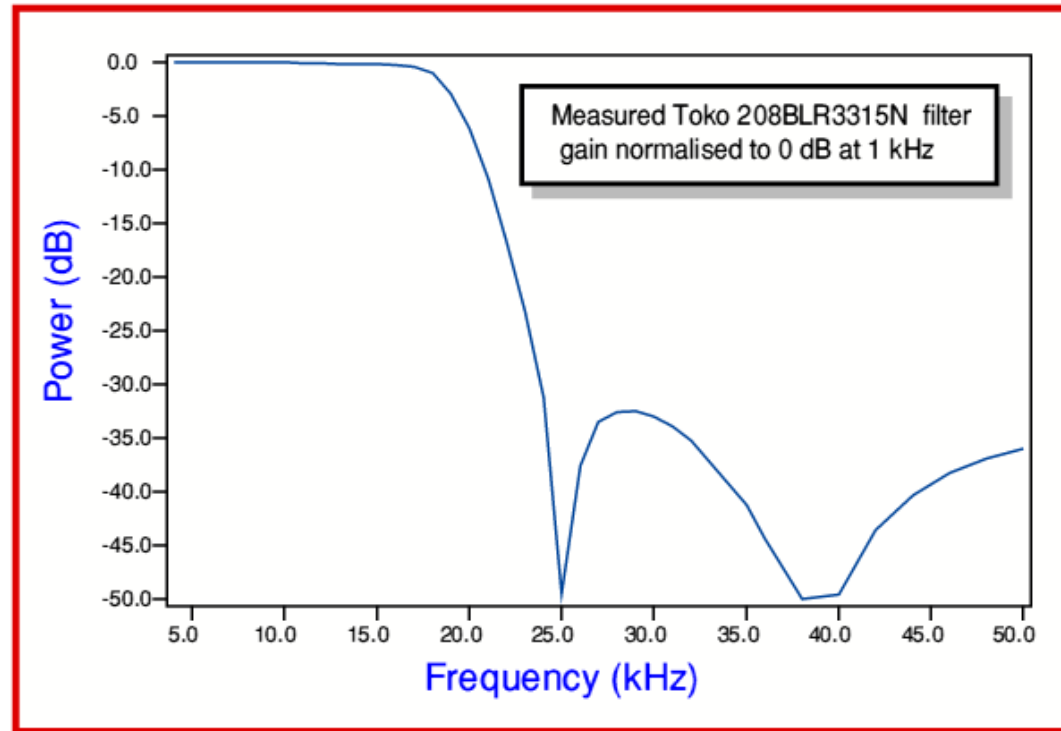


Mike Burnett's-Stereocoder

This schematic was originally drawn by [Mike Burnett](#) on 7th of February 1994. His drawings were scanned by someone else and the files were quite huge. So we took some time to re-draw them and you can see the result below. All chokes are type 8RB or 10RB. The audio lowpassfilters are Toko Type 208BLR3315N. The audioresponse of this filter and a loss compensating schematic are presented in the figure below (images come from [Scots Audio Guide](#))



Powered by a pair of PP3s this gives up to $\pm 6V$ out.
 Response approx 1 Hz to 16kHz (about -3dB points).
 Mid-band voltage gain around $\times 50$

